

DEVICES AND CIRCUITS LABORATORY  
EXPERIMENT-1  
**LED And Photodiode Characterizations**

Tanish H Talapaneni  
200020050

NGSPICE Code:


```
*DC_Lab_E1
Vin 1 0 dc=0
.dc Vin 0 5 0.2
R1 1 2 1k
R2 1 3 1k
R3 1 4 1k
d1 2 5 green
d2 3 6 red
d3 4 7 blue
vdummy1 5 0 0
vdummy2 6 0 0
vdummy3 7 0 0

.model red D(Vj=.75 Cjo=175p Rs=.25 Eg=3.2 M=.5516 Nbv=1.6989 N=2.4 Bv=1.7
Fc=.5 Ikf=0
Ibv=20.245m Is=880.5E-18)
.model green D(Is=1e-19 Rs=1.5 N=1.5 Cjo=50p Iave=30m Vpk=5)
.model blue D(IS=93.1P RS=42M N=7.47 BV=5 IBV=30U CJO=2.97P VJ=.75 M=.333
TT=4.32U)
.save all @d1[id]
.save all @d2[id]
.save all @d3[id]


.control
run
plot @d1[id] vs v(2,5),@d2[id] vs v(3,6),@d3[id] vs v(4,7)
plot ln(@d1[id]) vs v(2,5),ln(@d2[id]) vs v(3,6),ln(@d3[id]) vs v(4,7)

.endc
.end
```

Plot 1: Diode Current vs Diode Voltage

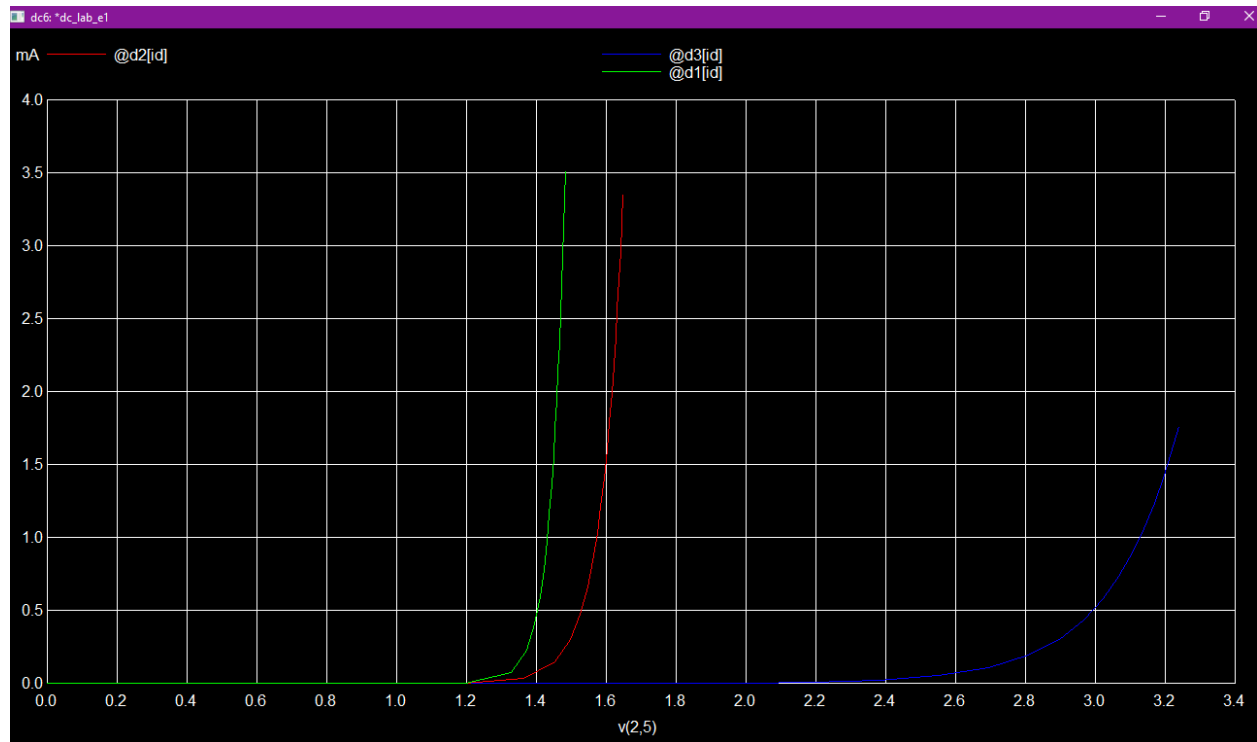

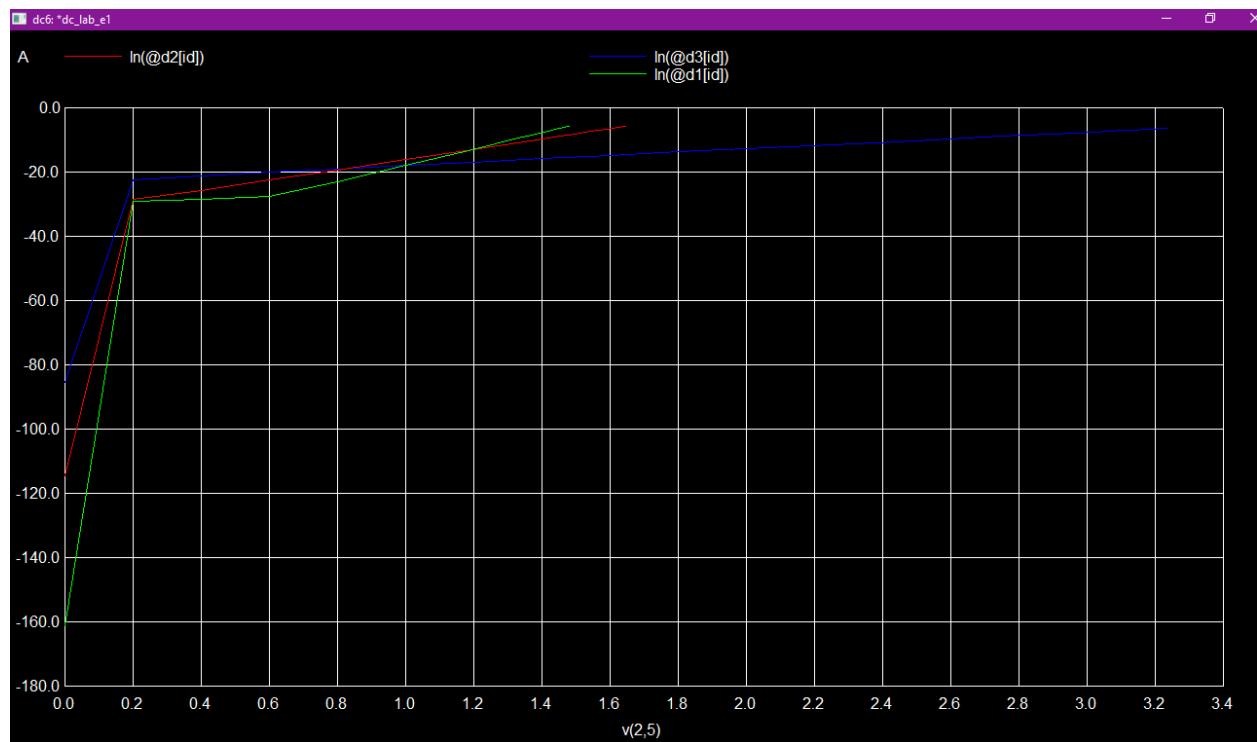Plot 2:  $\ln(\text{Diode Current})$  vs Diode Voltage




Observations:

14/12/21

LAB-1 SIMULATION  
REPORT

TANISHK.H.T  
200020050

CIRCUIT:-

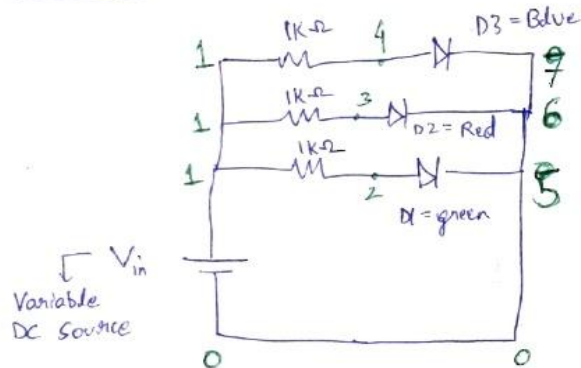

OBSERVATIONS:-

SATURATION CURRENTS:-  
(Approximate)

BLUE:- +50  $\mu A$

RED:- +20  $\mu A$

GREEN:- +80  $\mu A$

SLOPES of PLOT 2:- GREEN:- 650

RED:- 410

BLUE:- 325

Taking  $V_T = 25.85 mV$

The respective Ideality factors:-

RED:- 0.9435

BLUE:- 1.1903

GREEN:- 0.5951

Bandgap ( $E_g$ ):-

$$\text{BLUE:- } \frac{1240}{450} = 2.75 \text{ eV}$$

$$\text{RED:- } \frac{1240}{700} = 1.77 \text{ eV}$$

$$\text{GREEN:- } \frac{1240}{550} = 2.25 \text{ eV}$$


for  $I_D = 1 \text{ mA}$  :-

$$V_D \text{:- BLUE:- } 3.125 \text{ V}$$

$$\text{RED:- } 1.572 \text{ V}$$

$$\text{GREEN:- } 1.431 \text{ V}$$

$V_D$  vs  $E_g$  graph :-

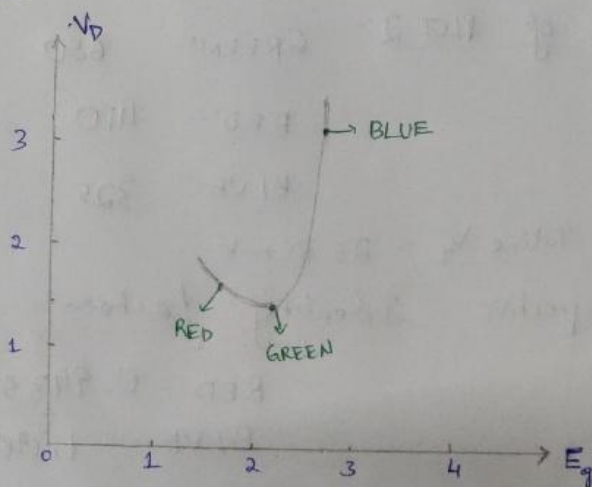

## Discussion:

### DISCUSSION:-

The saturation currents of the LED lights are very small, in the order of  $\mu A$  and goes in the order of  $\text{red} < \text{blue} < \text{green}$

The ideality factors of the given photodiodes indicate how close the behavior of the given diodes are, w.r.t to the ideal diode [Ideality factor  $\approx 1$ ] indicates that the <sup>given</sup> diode almost behaves like an ideal diode.

The Band-gap energy of each diode is indirectly proportional to the wavelength of light emitted by it. Since wavelength follows the order:  $\text{Blue} < \text{Green} < \text{Red}$ ; Band-gap energy follows the order  $\text{Blue} > \text{Green} > \text{Red}$ . Thus, the Red LED requires lesser energy to get excited compared to the blue & green LED.

Regarding  $V_D$ ,  $V_D$  (for  $I_D = 1 \text{ mA}$ ) for Blue is quite higher, compared to Red & green (almost double). The trend in  $V_D$  vs  $E_g$  graph indicates that, generally, with increase in  $E_g$ ,  $V_D$  tends to increase. i.e., more voltage is to be applied

across the photodiode, to obtain the same diode current, if the band-gap energy of the diode is higher.

### SCOPE FOR TECHNICAL IMPROVEMENT :-

- Since the saturation currents of the diodes are very low, they need to be measured with better accuracy.
  - The slopes need to be calculated efficiently from the plots obtained from NG Spice. The points on the graph should be chosen with better accuracy, and it is tough to obtain, using just a mouse-pointer.
- Thus, the ideality factors obtained may not be as accurate as we expect it to be.