

ED ASSIGNMENT-2

Tanish H Talapaneni
200020050

QUESTION 1

```
v1 1 0 dc=5
d1 1 2 D1N750
r1 2 0 1k
.model D1N750 D(Vj=.653 Cjo=175p Rs=.25 Eg=1.11 M=.5516 Nbv=1.6989 N=1 Bv=8.1 Fc=.5
lkf=0 lbv=20.245m ls=980.356E-20 Xti=3)
.save all @d1[id]
.dc v1 -10 5 0.05
* Control Statements
.control
run
*white background
set color0=white
* black grid and text
set color1=black
* wider grid and plot lines
set xbrushwidth=2
plot @d1[id] vs v(1)
.endc
.end
```

Q000200501
TANKHUT

ED ASSIGNMENT-2

Q1) (a) Built-in potential :-

$$\begin{aligned} V_0 &= V_T \ln \left(\frac{N_A N_D}{n_i^2} \right) \\ N_A &= 10^{15} / \text{cm}^3 &= \frac{kT}{q} \cdot \ln \left(\frac{N_A N_D}{n_i^2} \right) \\ N_D &= 2 \times 10^{16} / \text{cm}^3 &= \frac{1.38 \times 10^{-23} \times 300 \cdot \ln \left(\frac{2 \times 10^{31}}{2.25 \times 10^{20}} \right)}{1.6 \times 10^{-19}} \\ n_i &= 1.5 \times 10^{10} / \text{cm}^3 &= 0.0259 \left(11 \ln 10 + \ln(2/2.25) \right) \\ & &= 0.0259 \left(11(2.303) - 0.118 \right) \\ & &= 0.0259 (25.252) \\ & &\approx \boxed{0.653 \text{ V}} \end{aligned}$$

(b) Reverse Saturation current:-

$$J_s = e n_i^2 \left[\frac{1}{N_a} \sqrt{\frac{D_n}{\tau_{no}}} + \frac{1}{N_d} \sqrt{\frac{D_p}{\tau_{po}}} \right]$$
$$= 1.6 \times 10^{-19} \times 2.25 \times 10^{20} \left[\frac{1}{10^{16}} \sqrt{\frac{35}{5 \times 10^{-6}}} + \frac{1}{2 \times 10^{16}} \sqrt{\frac{12}{5 \times 10^{-6}}} \right]$$

$$\begin{aligned} D_n &= 35 \text{ cm}^2/\text{s} \\ D_p &= 12 \text{ cm}^2/\text{s} \\ \tau_{po} \text{ \& } \tau_{no} &= 5 \times 10^{-6} \text{ s} \end{aligned}$$


$$= 3.6 \times 10 \left[\frac{\sqrt{7}}{10^{12}} + \sqrt{\frac{3}{5}} \frac{1}{10^{13}} \right]$$
$$= 36 \left[2.646 \times 10^{-12} + 0.774 \times 10^{-13} \right]$$
$$= 36 \left[26.46 \times 10^{-13} + 0.774 \times 10^{-13} \right]$$
$$= 980.356 \times 10^{-13}$$

Now, Area:- $10 \mu\text{m}^2 = 10 \times 10^{-6} \text{ m}^2$

$$= (\sqrt{10} \times 10^{-3} \text{ m})^2$$
$$= (\sqrt{10} \times 10^{-3} \times 10^2 \text{ cm})^2$$
$$= 10 \times 10^{-8} \text{ cm}^2 = 10^{-7} \text{ cm}^2$$

$$\Rightarrow I_s = J_s \times \text{Area}$$

$$= 980.356 \times 10^{-20} \text{ A}$$

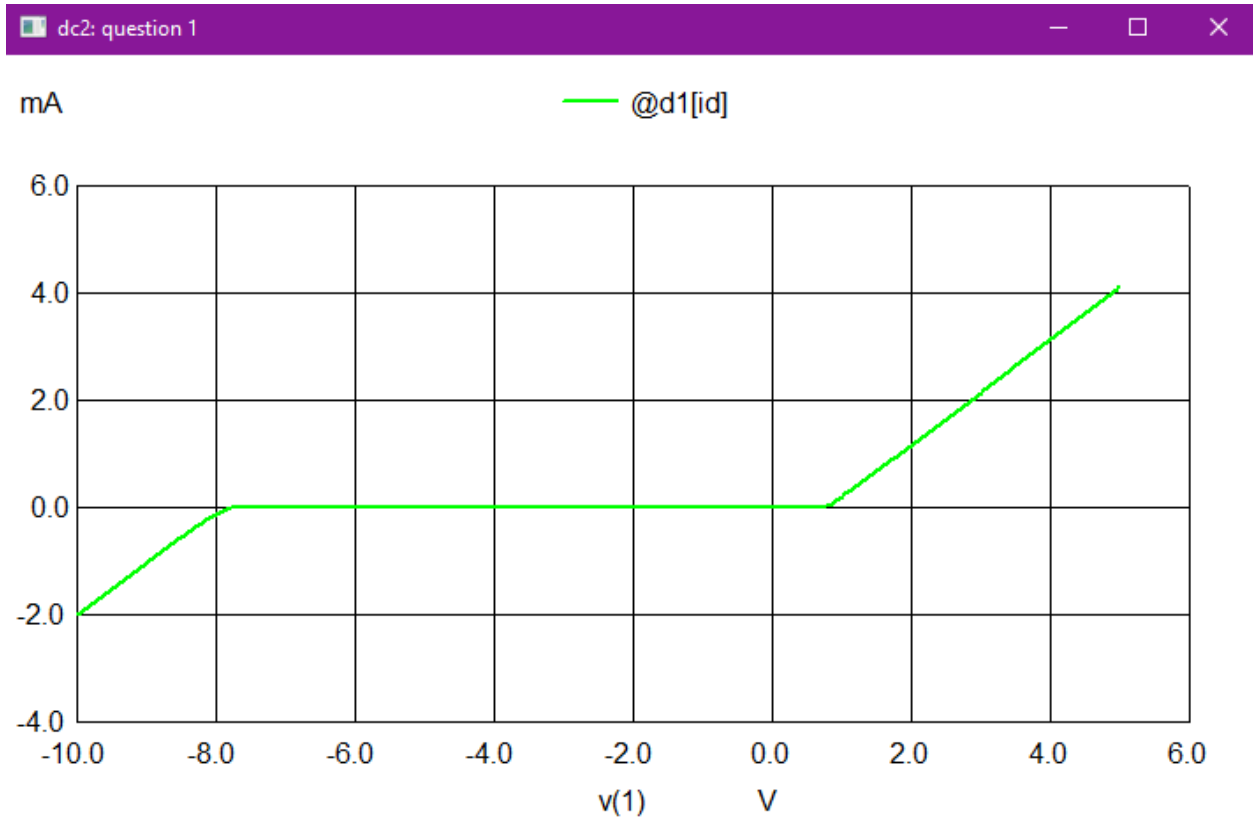

Interpretation:

The I-V Characteristics in the graph suggest that, roughly, the current is positive for positive voltage, and then, after a breakdown point, becomes negative. Under forward bias, the current is positive and is increasing as voltage is increasing, and under reverse bias, after the breakdown point, the current becomes more and more negative.

QUESTION 2

```
v1 1 0 dc=0 sin(0 5 200 0 0 0)
```

```
.ac lin 10 0.5 1Meg
```

```
.tran 0.05ms 25ms
```

```
v2 3 0 dc=2
```

```
d1 2 3 D1N750
```

```
r1 2 1 1000
```

```
.model D1N750 D(Vj=.653 Cjo=175p Rs=.25 Eg=1.11 M=.5516 Nbv=1.6989 N=1 Bv=8.1 Fc=.5
```

```
lkf=0 lbv=20.245m Is=980.356E-14 Xti=3)
```

```
* Control Statements
```

```
.control
```

```
run
```

```
*white background
```

```
set color0=white
```

```
* black grid and text
```

```
set color1=black
```


```
* wider grid and plot lines
```

```
set xbrushwidth=2
```

```
plot v(2) v(1)
```

```
.endc
```

```
.end
```

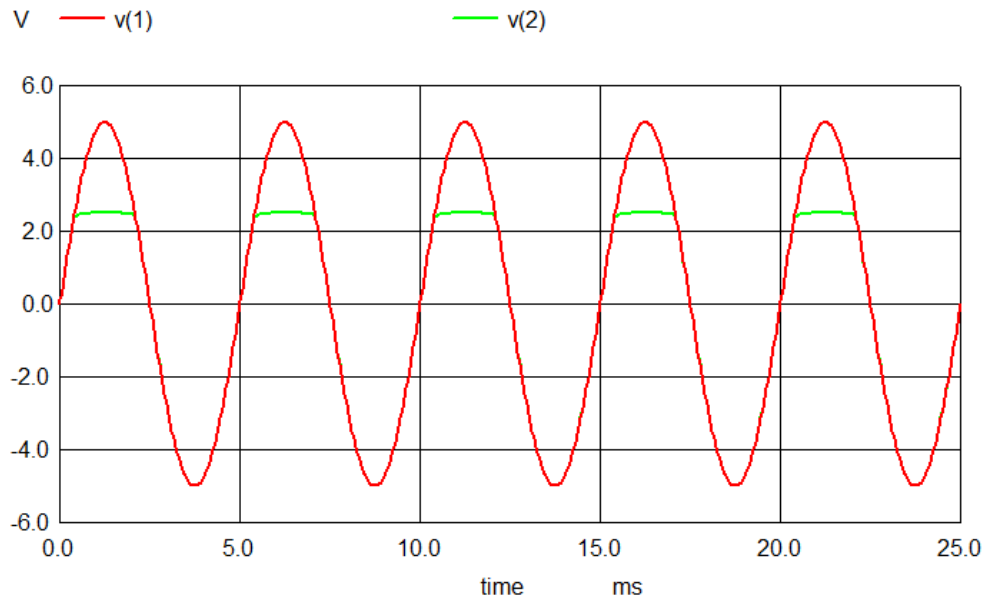

QUESTION 3A

```
v1 2 3 sin(0 2.5 1000 0 0 0)
```

```
.ac lin 10 0.5 1Meg
```

```
.tran 0.05ms 10ms
```

```
d1 0 2 D1N750
```

```
d2 2 4 D1N750
```

```
d3 0 3 D1N750
```

```
d4 3 4 D1N750
```

```
r1 4 0 1Meg
```

```
.model D1N750 D(Vj=.75 Cjo=175p Rs=.25 Eg=1.11 M=.5516 Nbv=1.6989 N=1 Bv=8.1 Fc=.5  
lkf=0 lbv=20.245m Is=880.5E-18 Xti=3)
```

```
* Control Statements
```

```
.control
```

```
run
```

```
*white background
```

```
set color0=white
```

```
* black grid and text
```

```
set color1=black
```


```
* wider grid and plot lines
```

```
set xbrushwidth=2
```

```
plot v(4) v(2,3)
```


```
.endc
```

```
.end
```

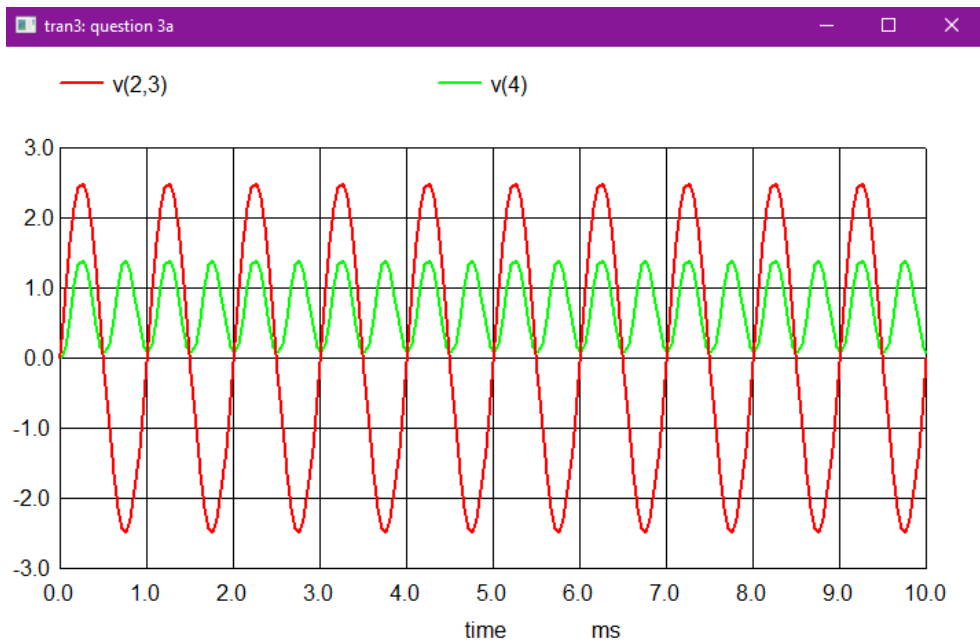

QUESTION 3B

```
v1 1 0 dc=-100
.dc v1 -150 -100 0.05
d1 0 2 D1N4148
r1 1 2 1000
r2 3 0 1Meg
.model D1N4148 D(Is=5.84n N=1.94 Rs=.7017 Ikf=44.17m Xti=3 Eg=1.11 Cjo=.95p+ M=.55
Vj=.75 Fc=.5 Isr=11.07n Nr=2.088 Bv=100 Ibv=100u Tt=11.07n)
* Control Statements
.control
run
*white background
set color0=white
* black grid and text
set color1=black
* wider grid and plot lines
set xbrushwidth=2
plot v(3) v(1)
.endc
.end
```

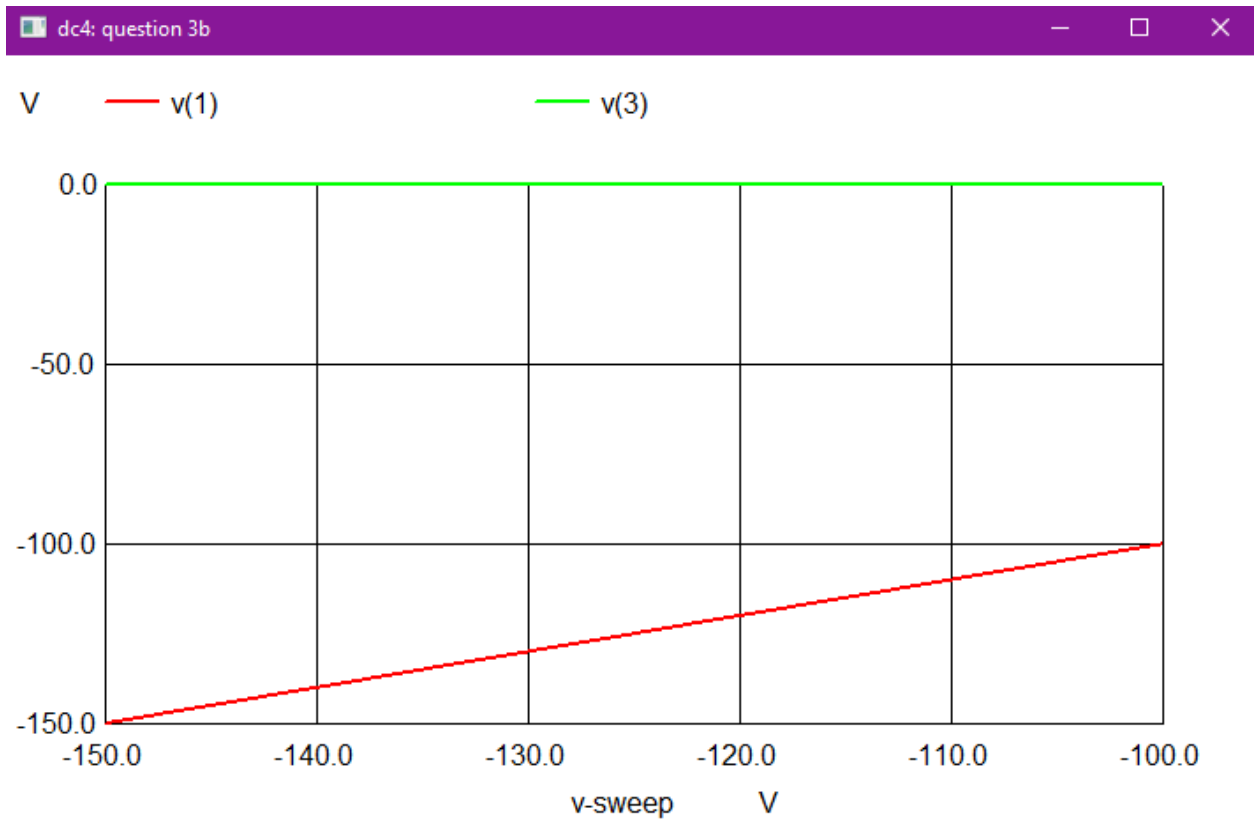

QUESTION 3C

```
v1 2 3 sin(0 2.5 1000 0 0 0)
```

```
.ac lin 10 0.5 1Meg
```

```
.tran 0.05ms 10ms
```

```
d1 0 2 D1N750
```

```
d2 2 5 D1N750
```

```
d3 0 3 D1N750
```

```
d4 3 5 D1N750
```

```
.model D1N750 D(Vj=.75 Cjo=175p Rs=.25 Eg=1.11 M=.5516 Nbv=1.6989 N=1 Bv=8.1 Fc=.5  
lkf=0 lbv=20.245m Is=880.5E-18 Xti=3)
```

```
v1 1 0 dc=-100
```

```
.dc v1 -150 -00 0.05
```

```
d1 0 5 D1N4148
```

```
r3 4 5 1000
```

```
r2 5 0 1Meg
```

```
.model D1N4148 D(Is=5.84n N=1.94 Rs=.7017 lkf=44.17m Xti=3 Eg=1.11 Cjo=.95p+ M=.55  
Vj=.75 Fc=.5 Isr=11.07n Nr=2.088 Bv=100 lbv=100u Tt=11.07n)
```

```
* Control Statements
```

```
.control
```

```
run
```

```
*white background
```

```
set color0=white
```

```
* black grid and text
```

```
set color1=black
```

```
* wider grid and plot lines
```

```
set xbrushwidth=2
```

```
plot v(5) v(2,3)
```

```
.endc
```

```
.end
```